



Cykel	Operation (RTN)	Aktiva styrsignaler
1	$12_{16} \rightarrow TA$	$OE_S, LD_{TA}$
2	$M(TA) \rightarrow T$	$MR, LD_T$
3	$13_{16} \rightarrow TA$	$OE_S, LD_{TA}$
4	$M(TA) + T \rightarrow R$	$MR, LD_R, F(1011),$
5	$14_{16} \rightarrow TA$	$OE_S, LD_{TA}$
6	$R \rightarrow M(TA)$	$OE_R, MW$